

# AC electric circuits


## Quick introduction to complex numbers

Alternating current circuits can be solved with the same tricks used for DC circuits, but they are a bit different.

While in DC circuits all quantities are just real numbers, in AC circuits we have to operate with **complex numbers**, also called **vectors**.

Basically a complex number is a binomial expression made of a **real part** (*just a number*) and an **imaginary part**, which is a multiple of the imaginary unit **j**, so called because it is the square root of -1 (*nonsense in real numbers*).

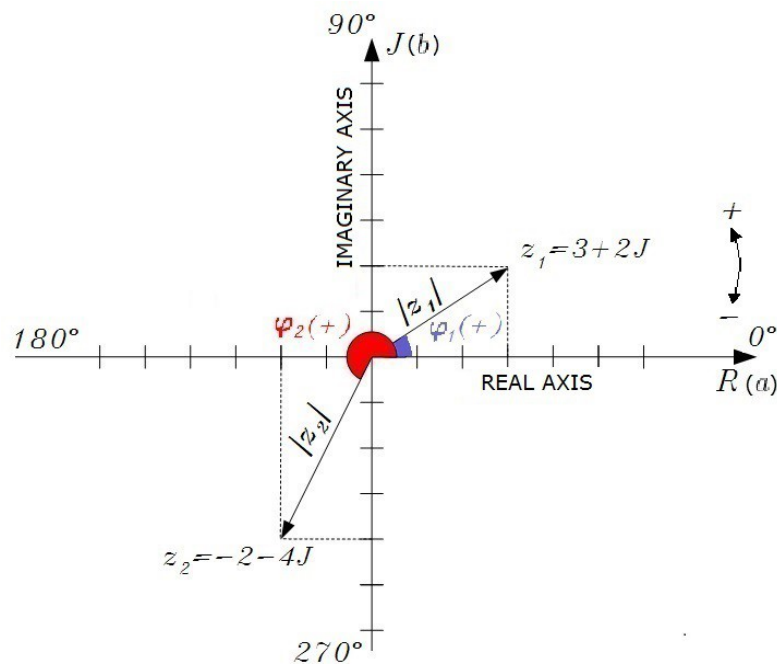Complex numbers can be represented graphically on the vector compass, which is made of a real horizontal axis and an imaginary vertical axis.



$$|z| = \sqrt{a^2 + b^2} \quad z = a + bJ$$

$$J = \sqrt{-1} \quad J^2 = -1$$

$$\cos\varphi = \frac{a}{|z|} \quad \sin\varphi = \frac{b}{|z|}$$

$|z|$  = length or modulus

$\varphi$  = angle

They can be converted from the binomial to the polar form (*length, angle*) and vice-versa by the Pythagorean Theorem or the trigonometry.

As binomial expressions complex numbers can be added, subtracted, multiplied and divided, but we have to assume that  $\mathbf{j^2 = -1}$ .

In the following division both quantities are multiplied by the **complex conjugate** of the denominator, which becomes a real number:

$$\begin{aligned}\frac{3 + 2j}{2 - 3j} &= \frac{(3 + 2j)(2 + 3j)}{(2 - 3j)(2 + 3j)} = \frac{6 + 9j + 4j + 6j^2}{4 + 6j - 6j - 9j^2} = \\ &= \frac{6 + 13j + 6(-1)}{4 - 9(-1)} = \frac{6 + 13j - 6}{4 + 9} = \frac{13j}{13} = j\end{aligned}$$

## Impedance

It is analogue to the resistance in a DC circuit.

The impedance of an AC circuit is represented by a vector (*usually indicated with the letter z*).

The real part is related to the resistance; it is always positive.

The imaginary part is related to the capacitive or inductive reactance.

An impedance can be pure resistive, pure capacitive, pure inductive or mixed.

### **Pure resistive**

The vector features a positive real part, which is related to the resistance.

$$Z_R = R$$

### **Pure capacitive**

$$X_C = \frac{1}{2\pi fC} \quad Z_c = -X_C j$$

The vector is only made of a negative imaginary part and the coefficient corresponds to the reactance of the capacitor.

$$X_C = \text{capacitive reactance } [\Omega] \quad C = \text{capacitance } [F] \quad f = \text{frequency } [Hz]$$

## Pure inductive

The vector is only made of a positive imaginary part and the coefficient corresponds to the reactance of the inductor.



$$X_L = 2\pi fL \quad Z_L = X_L j$$

$X_L$  = inductive reactance [ $\Omega$ ]     $L$  = inductance [H]

## Equivalent impedance

Series:  $Z_{EQ} = Z_1 + Z_2$     Parallel:  $Z_{EQ} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2}$

The example below shows a RLC series:

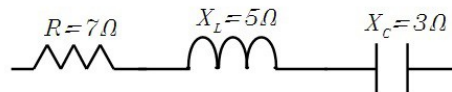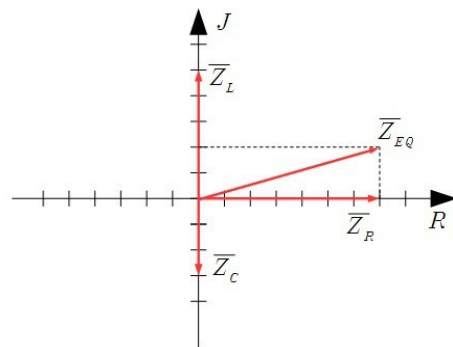

$$Z_R = 7$$

$$Z_L = 5j$$

$$Z_C = -3j$$

$$Z_{EQ} = Z_R + Z_L + Z_C = 7 + 5j - 3j = 7 + 2j$$

$Z_{EQ}$  = series equivalent impedance

# AC voltage and current

Voltage and current are alternating quantities, whose variation is represented by a **sine wave**, related to a **rotating vector**. This one spins with an angular speed associated with the frequency.

$$\omega = 2\pi f$$


$$\omega = \text{angular speed [radians/second]}$$

$$2\pi \text{ radians} = 360^\circ$$


$$f = \text{frequency [Hz; spins/second]}$$

The imaginary part of the vector corresponds to **instantaneous value** of the sine wave, while the modulus (*which is constant*) corresponds to the **peak value**, that is positive at  $90^\circ$  and negative at  $270^\circ$ .

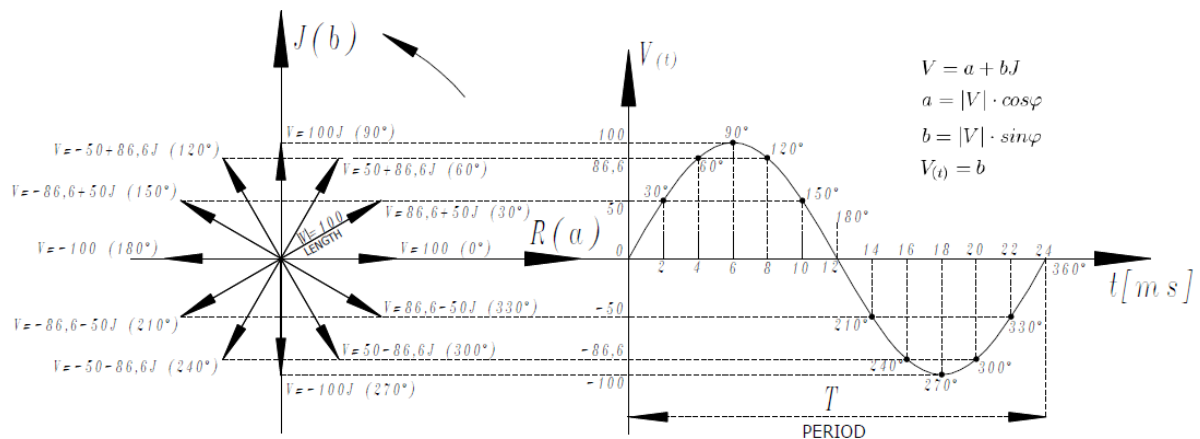The example below is about a voltage of 100 V. The vector performs a rotation of  $360^\circ$  in 24 milliseconds, so the frequency is 41,7 Hz ( $f=1/T$ ).



## How to solve AC circuits

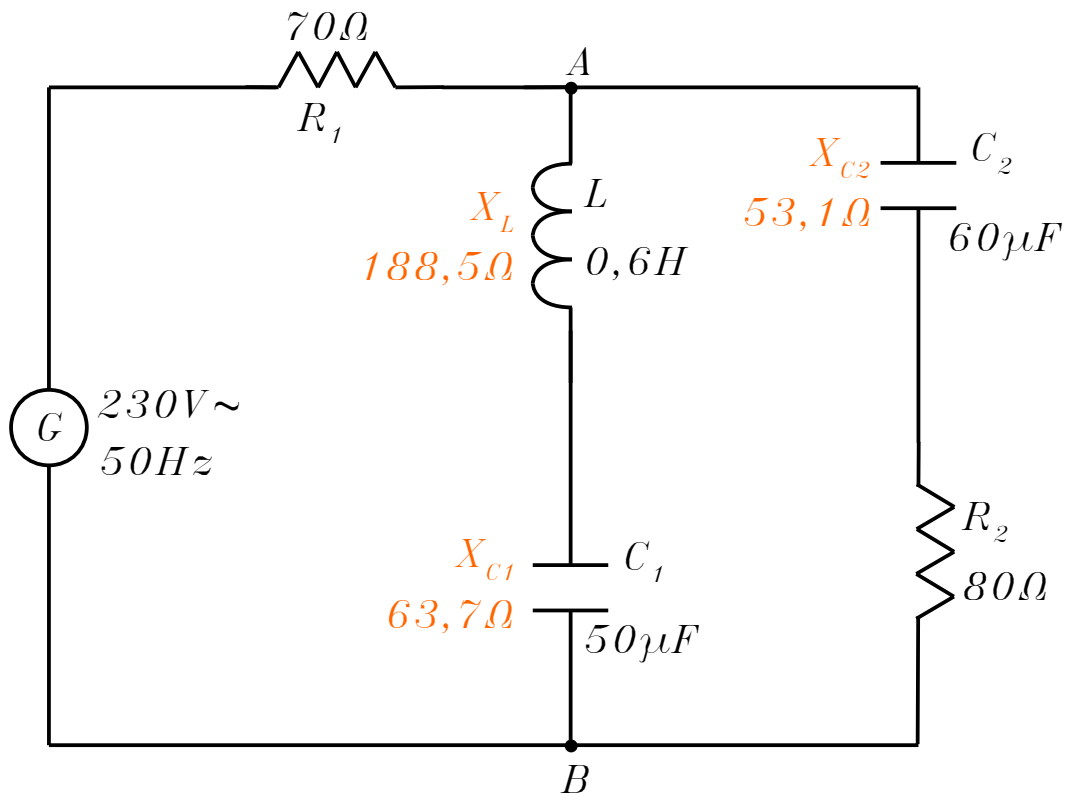

All first we have to calculate inductive and capacitive reactances ( $X_L$ ,  $X_C$ ):

$$X_L = 2\pi fL = 2\pi * 50 * 0,6 = 188,5\Omega$$

$$X_{C1} = \frac{1}{2\pi fC_1} = \frac{1}{2\pi * 50 * 50 * 10^{-6}} = 63,7\Omega$$

$$X_{C2} = \frac{1}{2\pi fC_2} = \frac{1}{2\pi * 50 * 60 * 10^{-6}} = 53,1\Omega$$

$$Z_{R1} = 70$$

$$Z_L = 188,5j$$

$$Z_{C1} = -63,7j$$

$$Z_{C2} = -53,1j$$

$$Z_{R2} = 80$$

$$|Z_R| = R$$

$$|Z_C| = X_C$$

$$|Z_L| = X_L$$


Since we use current and voltage divider we have to calculate the equivalent impedance.

$Z_{C2}$  is connected in series with  $Z_{R2}$ , while  $Z_L$  is connected in series with  $Z_{C1}$ :

$$Z_{S1} = Z_{C2} + Z_{R2} = 80 - 53,1j \quad |Z_{S1}| = \sqrt{80^2 + 53,1^2} = 96\Omega$$

$$Z_{S2} = Z_L + Z_{C1} = 188,5j - 63,7j = 124,8j$$

$$|Z_{S2}| = 124,8\Omega$$

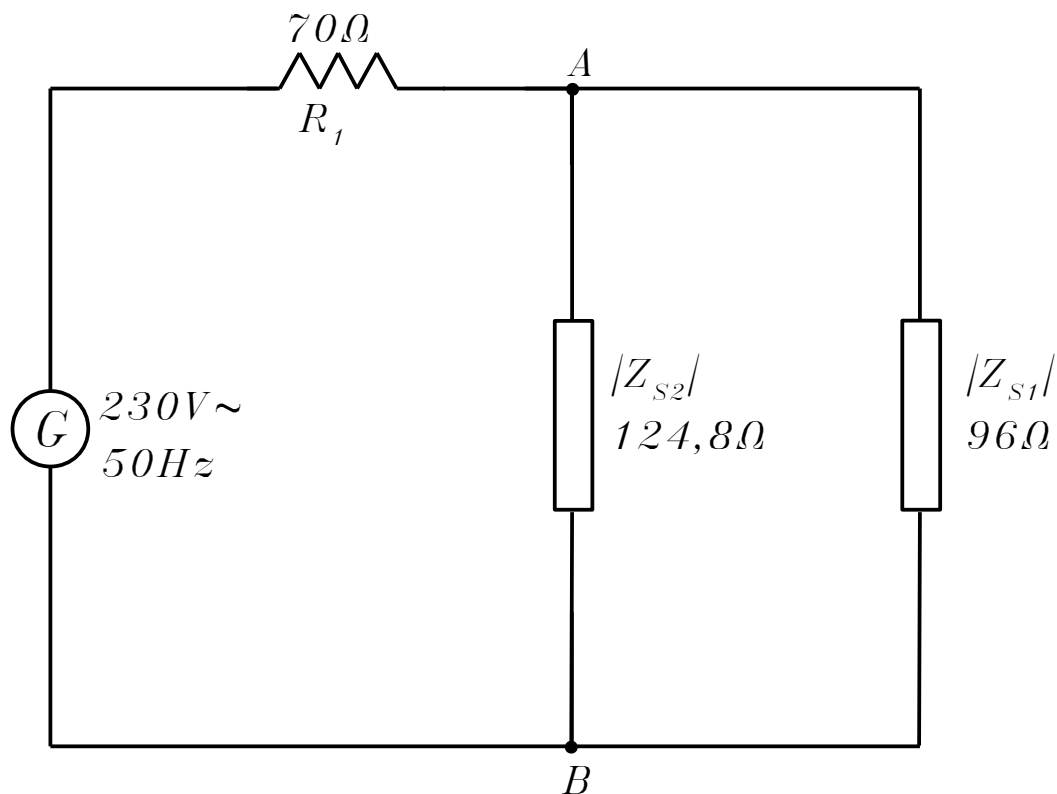

$Z_{S1}$  and  $Z_{S2}$  are connected in parallel:


$$Z_P = \frac{Z_{S1} * Z_{S2}}{\overline{Z_{S1}} + \overline{Z_{S2}}} = \frac{(80-53,1J)*124,8J}{80-53,1J+124,8J} = 108+28J$$

$$|Z_P| = \sqrt{108^2 + 28^2} = 111,5\Omega$$

$Z_P$  and  $Z_{R1}$  are connected in series:

$$Z_{EQ} = Z_{R1} + Z_P = 70 + 108 + 28J = 178 + 28J$$

$$|Z_{EQ}| = \sqrt{178^2 + 28^2} = 180,2\Omega$$

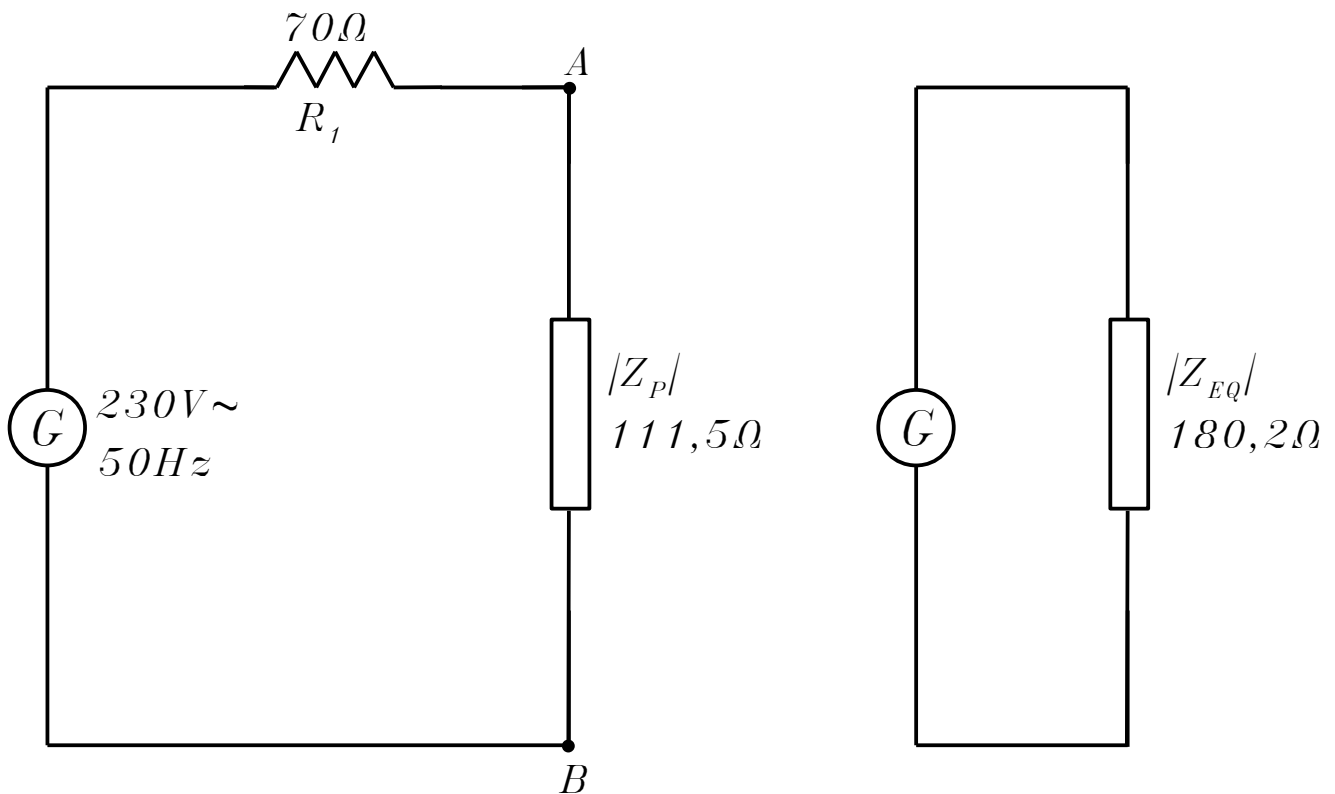


While a vector related to impedance features a constant position, a vector related to voltage or current rotates on the axes intersection. Since we start from the source  $V_G$ , we have to choose at will the position that the vector  $V_G$  assumes at the instant  $t_0$ . By using Ohm's and Kirchhoff's law with complex numbers we can calculate the currents flowing through the circuit at the instant  $t_0$ .

$$|V_G| = 230V \quad (\text{peak value} = \pm 230V) \quad \varphi_{VG} = 60^\circ \quad V_G = a + bJ$$

$$a = |V_G| \cdot \cos \varphi = 230 \cdot \cos 60^\circ = 115$$

$$b = |V_G| \cdot \sin \varphi = 230 \cdot \sin 60^\circ = 199,2$$
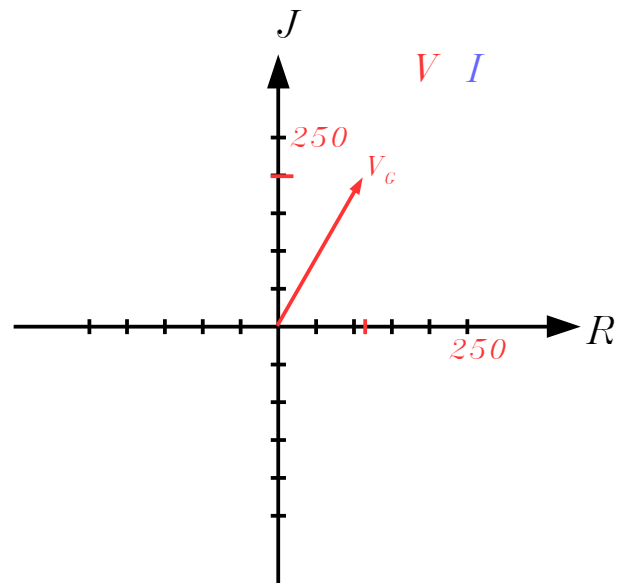
$$V_G = 115 + 199,2J \quad V_{G(t)} = 199,2V$$



At the instant  $t_0$  the voltage  $V_G$  features  $60^\circ$  (chosen at will) and  $199,2V$ . Using Ohm's Law:


$$I_G = \frac{V_G}{Z_{EQ}} = \frac{115 + 199,2J}{178 + 28J} = 0,8 + 0,99J \quad I_{G(t)} = 0,99A$$

$$|I_G| = \sqrt{0,8^2 + 0,99^2} = 1,27A$$

$$\cos \varphi_{IG} = \frac{0,8}{1,27} = 0,63$$

$$\sin \varphi_{IG} = \frac{0,99}{1,27} = 0,78$$

$$\varphi_{IG} = 51^\circ$$

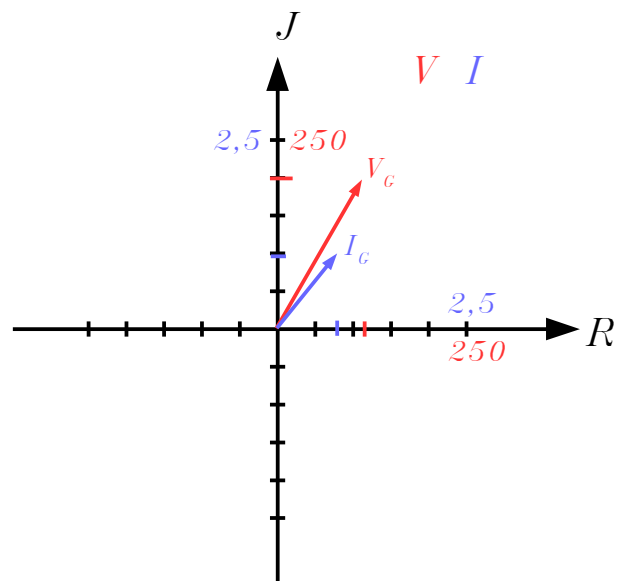

At the instant  $t_0$  the current  $I_G$  features  $51^\circ$  and  $0,99A$

The peak value of the current  $I_G$  (at  $90^\circ$  and  $270^\circ$ ) is  $\pm 1,27A$




Using voltage divider:

$$V_{AB} = I_G * Z_P = (0,8 + 0,99j) * (108 + 28j) = 58,7 + 129,3j$$

$$V_{AB(t)} = 129,3V$$

$$|V_{AB}| = 142V \quad \varphi_{VAB} = 65,6^\circ$$

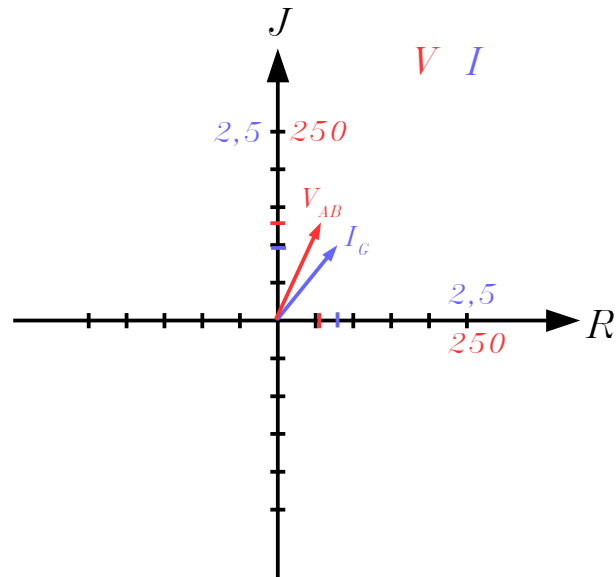


$$I_1 = \frac{V_{AB}}{Z_{S1}} = \frac{58,7 + 129,3j}{80 - 53,1j} = -0,24 + 1,46j \quad I_{1(t)} = 1,46A$$

$$|I_1| = 1,48A \quad \varphi_{I1} = 99,2^\circ$$

$$I_2 = \frac{V_{AB}}{Z_{S2}} = \frac{58,7 + 129,3j}{124,8j} = 1,04 - 0,47j \quad I_{2(t)} = -0,47A$$

$$|I_2| = 1,14A \quad \varphi_{I2} = -24,4^\circ$$

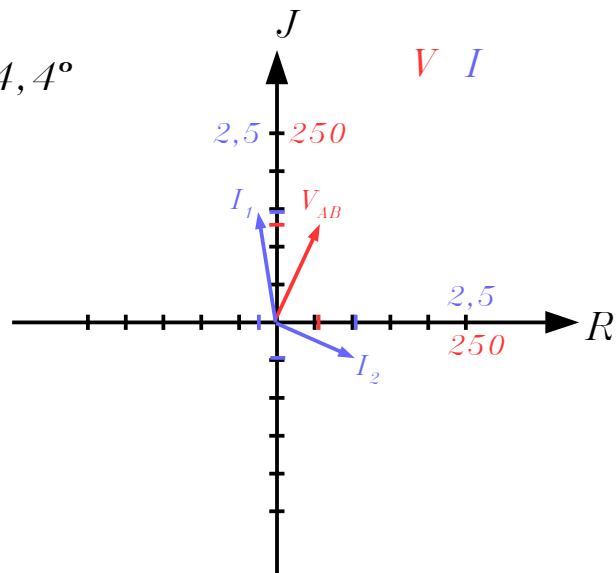

The direction of the currents can be chosen at will, but we have to respect Kirchhoff's current law:  $0,99A + 0,47A = 1,46A$

The schematic below shows the currents at the instant  $t_0$ :

